

HEADLIGHT WARNING ALARM


DIY - \$3

- Never leave your headlights on again
- a -Do It Yourself- (DIY) plug-in device
- Sounds an alarm if you leave your lights on
- Plug into the fuse block behind the glove box
- draws no power
- Works with old and new fuse blocks
-

PARTS NEEDED

\$3


TERMINAL (2)

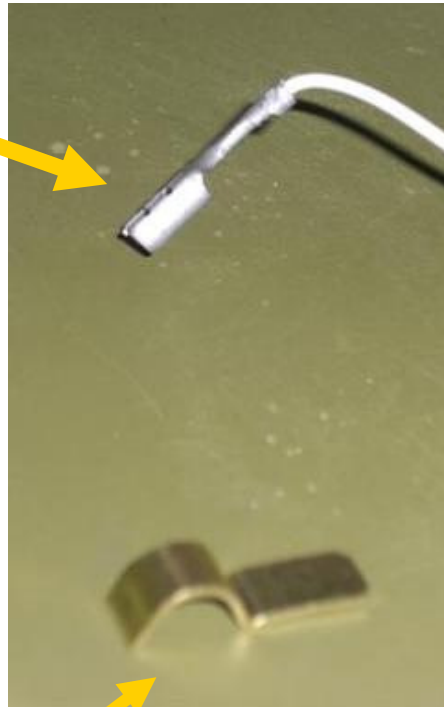


FUSE TAP (2)



NEW FUSE BLOCK

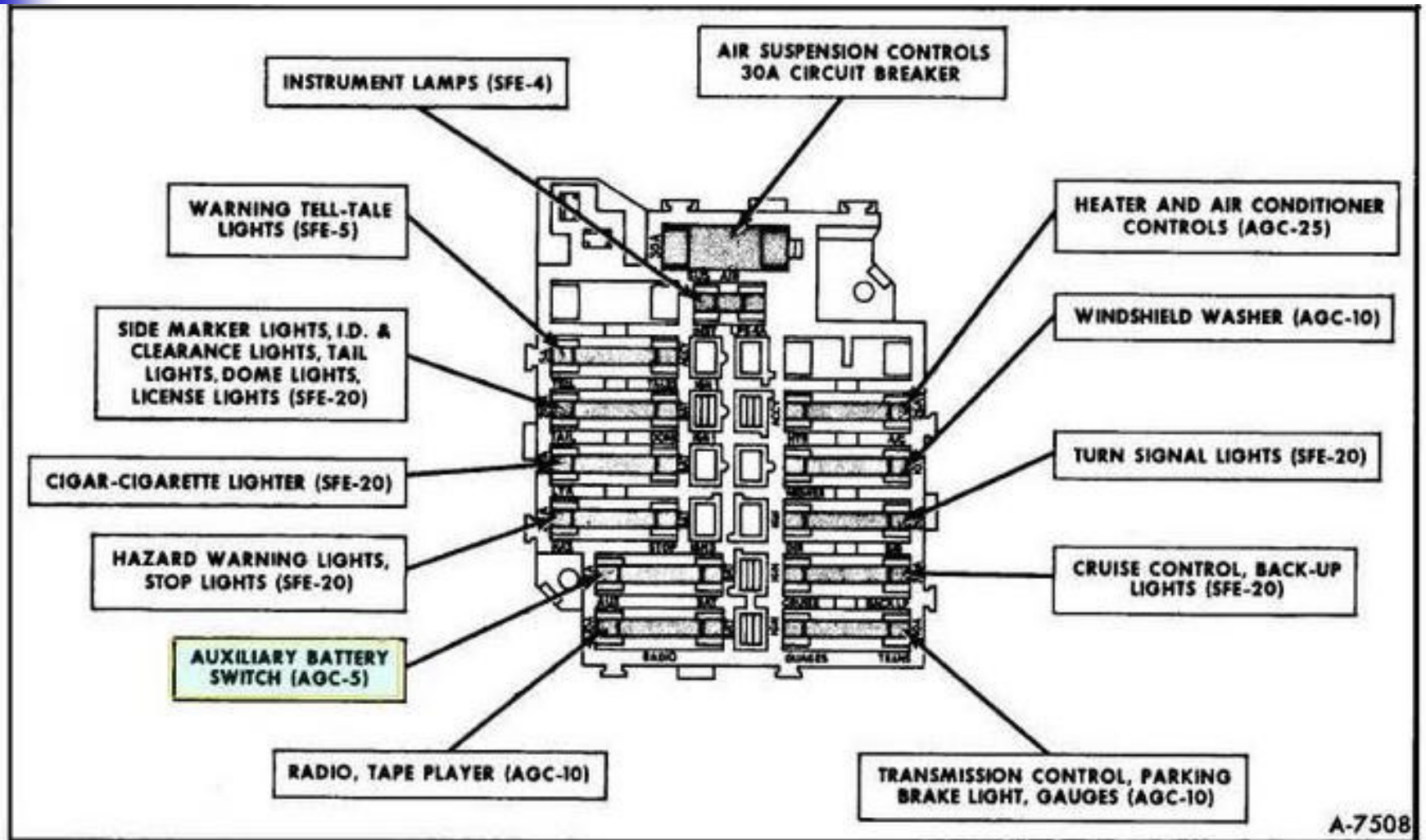

NEW FUSE BLOCK CONNECTIONS

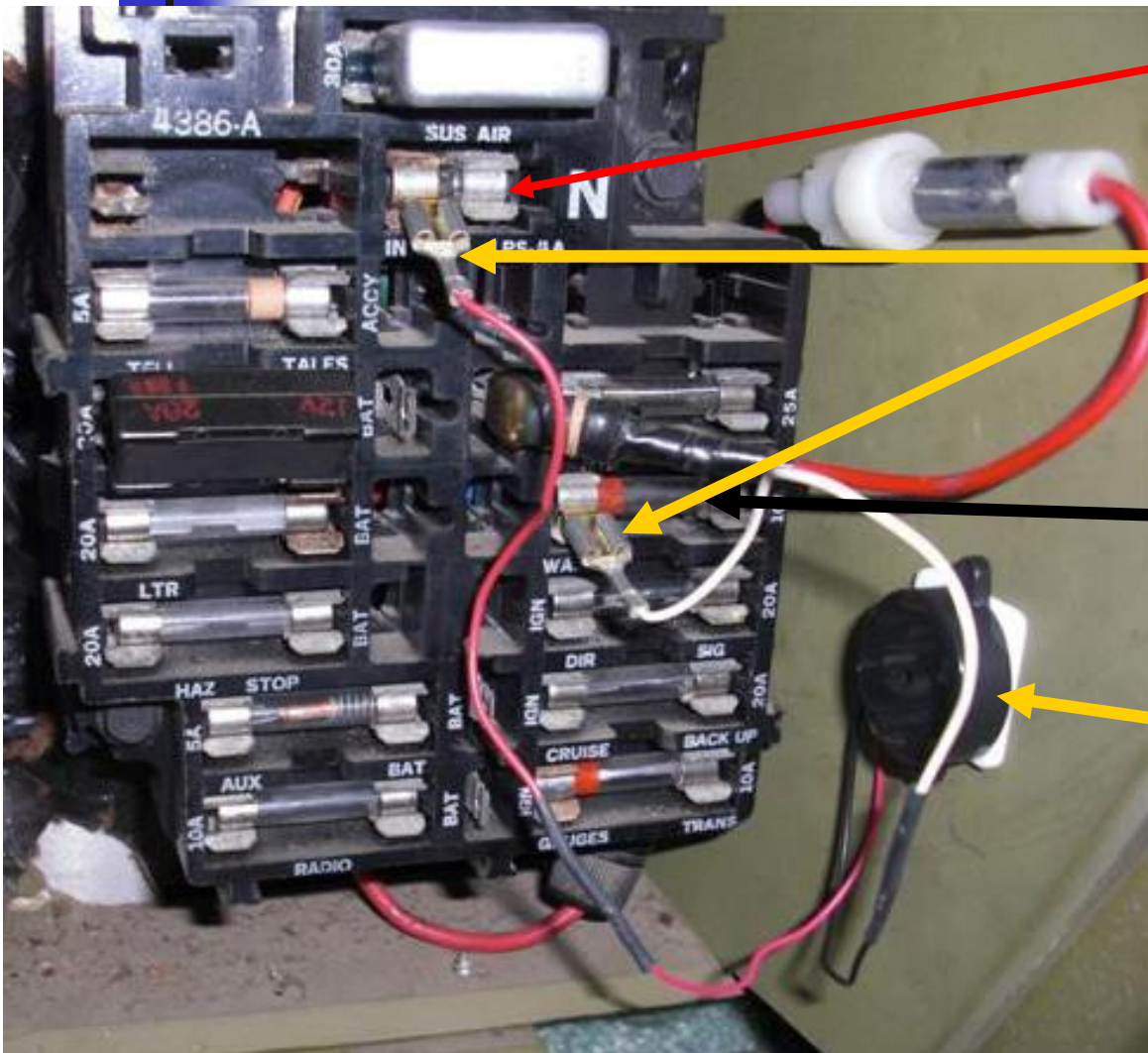


Positive - (red) to here

Fuse taps and terminals

Negative -(black or white)

Sonalert - Piezo Buzzer

OLD FUSE BLOCK

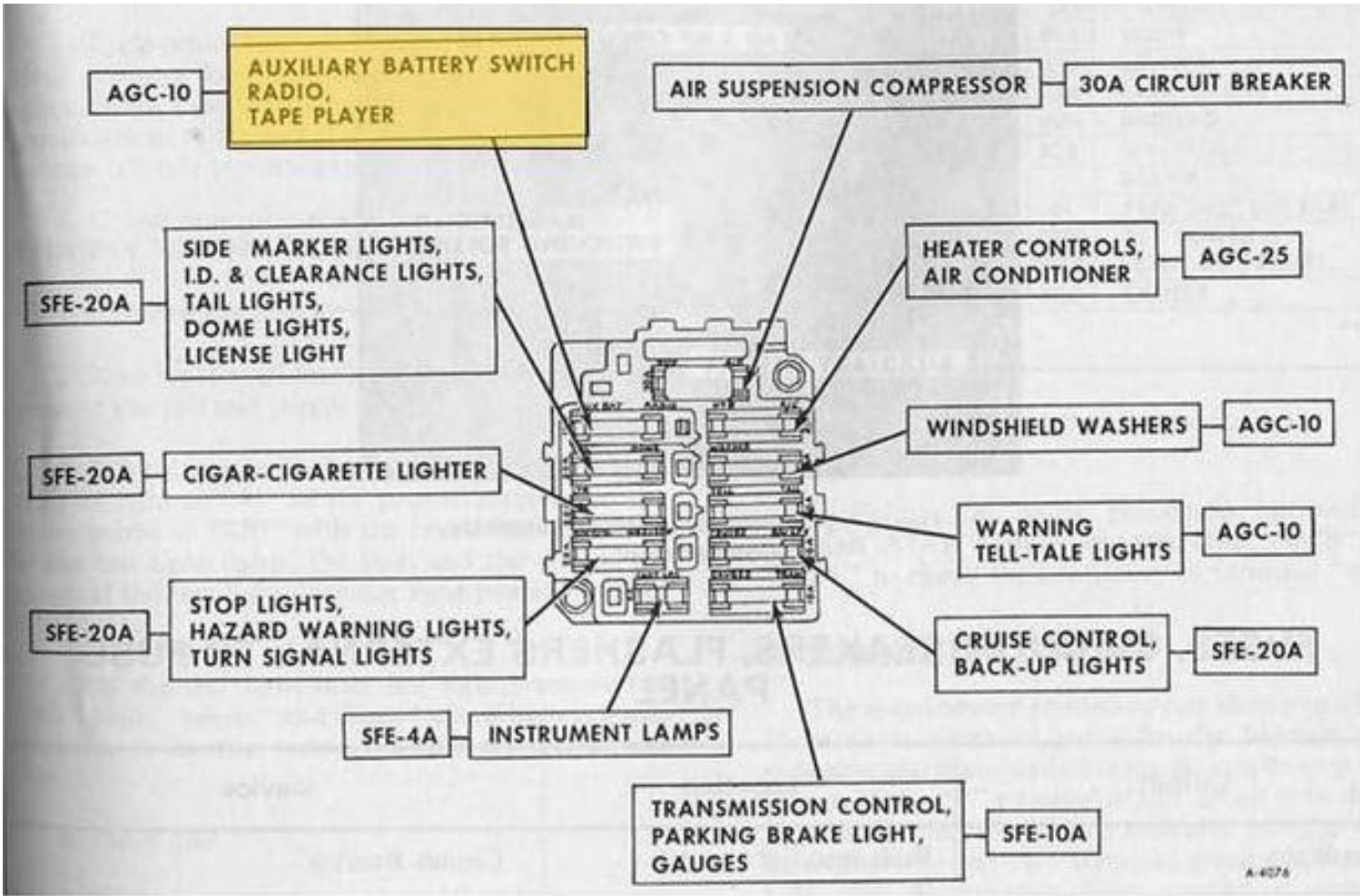

OLD FUSE BLOCK CONNECTIONS

